

电子科技大学 2020-2021 学年第 一 学期期末考试 A 卷

考试科目: 数字逻辑设计及应用 考试形式: 闭卷 考试日期: 2021 年 1 月 14 日

本试卷由 六 部分构成, 共 7 页。考试时长: 120 分钟

成绩构成比例: 平时成绩 60 %, 期末成绩 40 %

(可以使用中文解答; 禁止使用计算器; 题中所用器件功能表见试卷后附录 (Appendix))

题号	I	II	III	IV	V	VI	合计
得分							

得分

I. Please put the correct answers in the brackets “()”. (3' X 8 = 24')

1. A sequential circuit with 4 flip-flops can store (16) states at most.
2. A modulo-288 counter circuit can be built by (3) 4-bit counters of 74x163 at least.
3. To design a "001010" serial sequence generator by shift registers, (4) flip-flops are required at least.
4. There is a state transition equation $Q^*=JQ'+K'Q$. If we use a D flip-flop for state memory, the D input of the D flip-flop can be given as: $D = (JQ'+K'Q)$.
5. An n -bit Johnson counter has (2^n-2n) abnormal states.
6. Two common types of ripple counter are ripple up counter and ripple down counter. The circuit shown in Figure 1-1 is a 2-bit ripple (up) counter.
7. A 74x194 can be used as a sequence detector. When Z shown in Figure 1-2 is asserted, the sequence detected is (10110).

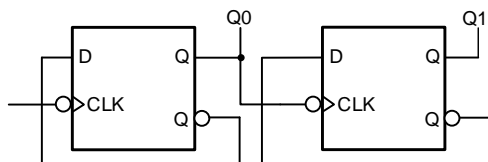


Figure 1-1

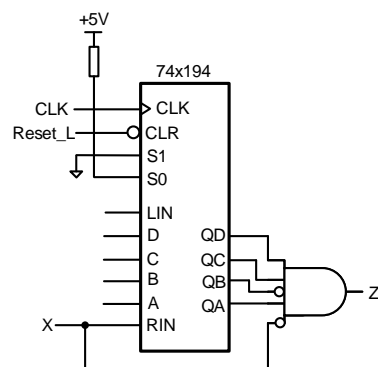


Figure 1-2

8. If a ROM has 13 address inputs and 8 data outputs, its capacity is (8)Kbyte.

得分

**II. Choose the correct answer and put the item number in the brackets.
(3' X 5=15')**

- Which of the following statements is correct? (A)
 - Both outputs of Mealy and Moore machine depend on states.
 - The outputs of a Mealy machine depend only on the states.
 - The outputs of a Moore machine depend on the inputs and states.
 - Both outputs of Mealy and Moore machine depend on inputs.
- A temperature test system whose temperature measurement range is $-45^{\circ}\text{C} \sim 125^{\circ}\text{C}$. If the A/D converter in the system needs to recognize a temperature change of 0.1°C , an A/D converter with (B) bits is required at least.

A. 10 B. 11 C. 12 D. 13
- A logic diagram is shown in Figure 2 and the current state $Q_3Q_2Q_1Q_0=1111$. If the CONTROL terminal is connected to HIGH level and LOW level respectively, the next state $Q_3^*Q_2^*Q_1^*Q_0^*$ should be (C).

A. 0000 and 1111 B. 1111 and 0000
C. 0000 and 0000 D. 1111 and 1111
- A 4×4 unsigned binary multiplication can be built with a (D) ROM.

A. 128×4 B. 256×4
C. 128×16 D. 256×8

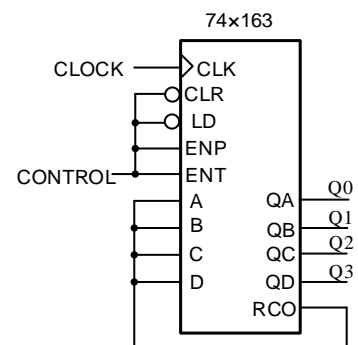


Figure 2

5. In the following circuits, only (C) is a sequential

logic

circuit.

- A. Three-State Buffers B. Comparators C. shift registers D. Decoders

得分

III. Analyze the sequential circuit shown in Figure3-1. (10')

- (1) Assuming the initial state $Q_1Q_2=00$, draw the timing diagrams for Q_1 , Q_2 and Z shown in Figure 3-2. [7']
- (2) According to the frequencies of the waveforms in Figure 3-2, what is the relation between Z and CLK ? [3']


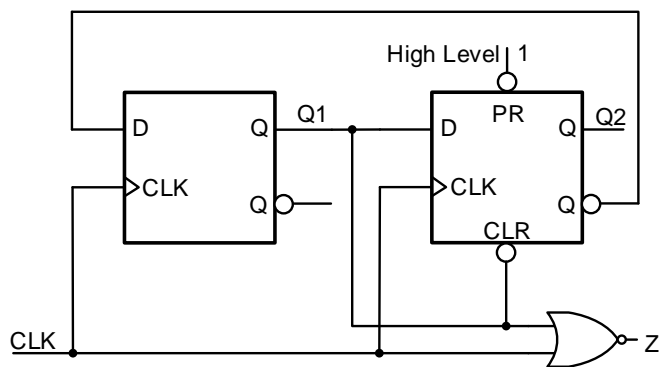


Figure 3-1

清零信号是否需要按照异步复位和同步复位两种情况分别考虑？（这道题没有明确提出是异步复位）

答案及参考评分：

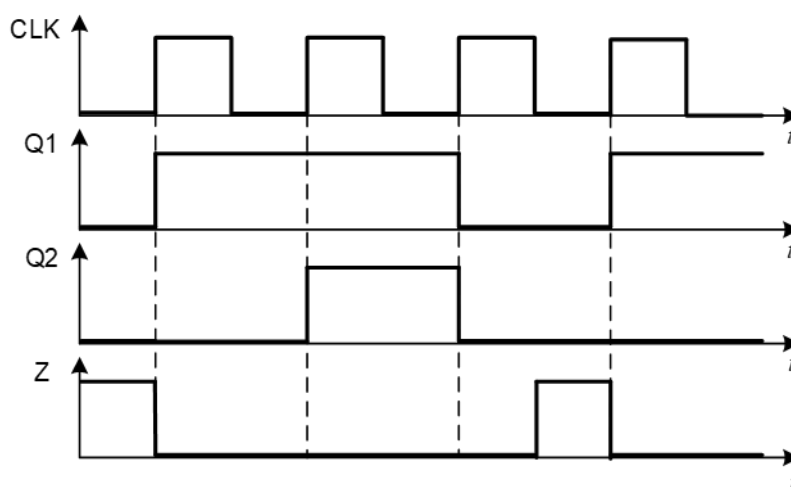- (1) 从 CLK 的第一个上升沿开始，波形 Q_1 , Q_2 , Z 各 2 分（每时钟周期错误扣 0.5 分），共 6 分；初始段 Z 正确给 1 分
- (2) Z 对 CLK 进行 3 分频。回答正确 3 分。



得分

IV. Analyze the sequential circuit shown in Figure 4. (17')

- (1) Draw the state diagram of the sequential circuit whose state is QD QC QB QA. [16']
- (2) According to the state diagram obtained from above, is the sequential circuit self-correcting or not? (yes/self-correcting/自校正/自启动/) [1']


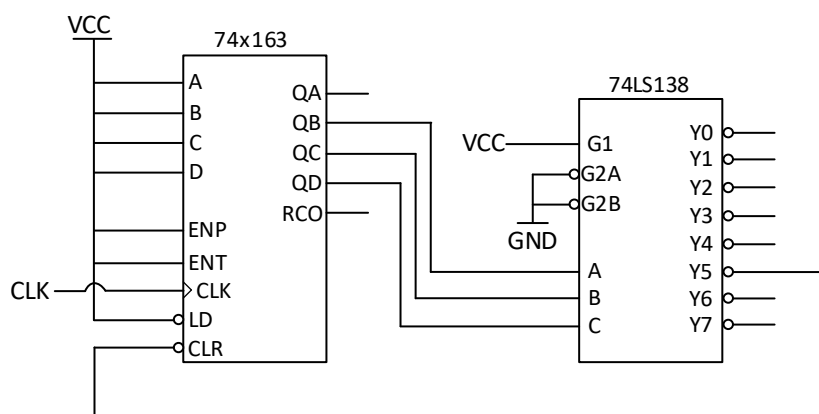


Figure 4

QD QC QB QA

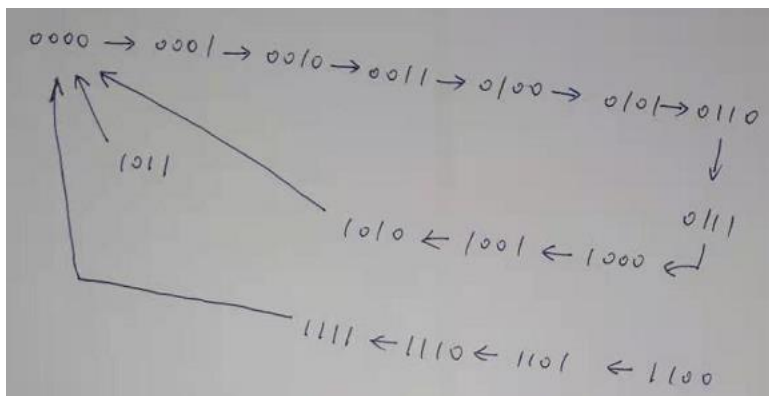

每个状态位置正确给 1 分。

得分

V. Design a clocked synchronous state machine with D flip-flops to obtain the output waveforms shown in Figure 5, where Q2, Q1 and Q0 are outputs of D flop-flops. (16')

- (1) Give the transition table of the state machine based on Figure 5. (choose the approach of minimal cost for unused states). [6']
- (2) List the unused states $Q_2Q_1Q_0$ and their next states $Q_2^*Q_1^*Q_0^*$ to show that whether or not the circuit is self-correcting. [5']
- (3) Give the logic diagram. [5']

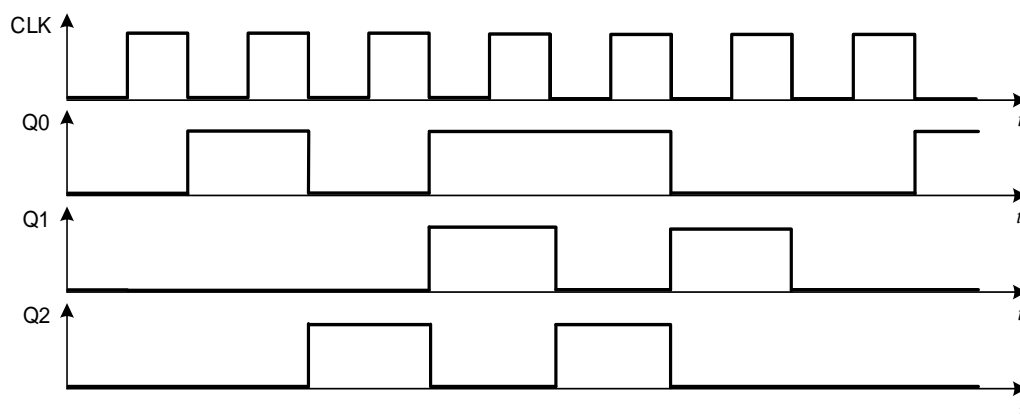


Figure 5


(1)

Q_2^*		Q_1^*	
Q_2Q_1		Q_2Q_1	
Q_0	0 0 0 1 1 1 1 0	Q_0	0 0 0 1 1 1 1 0
0	0 0 0 d 0	0	0 0 0 d 1
1	1 1 d 0	1	0 0 d 1

Q_0^*	
Q_2Q_1	
Q_0	0 0 0 1 1 1 1 0
0	0 1 0 d 1
1	0 1 d 0

每个状态转换表正确给 2 分；


(2)

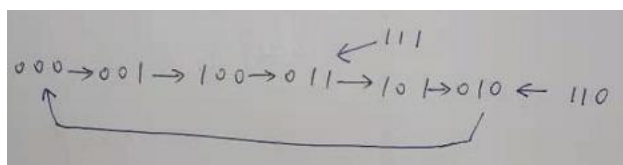

具有自校正功能。

正确给出 011、111 之间的状态关系得 1 分；010、110 之间的状态关系得 1 分；
回答出具有自校正功能给 1 分；正确画出状态图其他部分得 2 分。

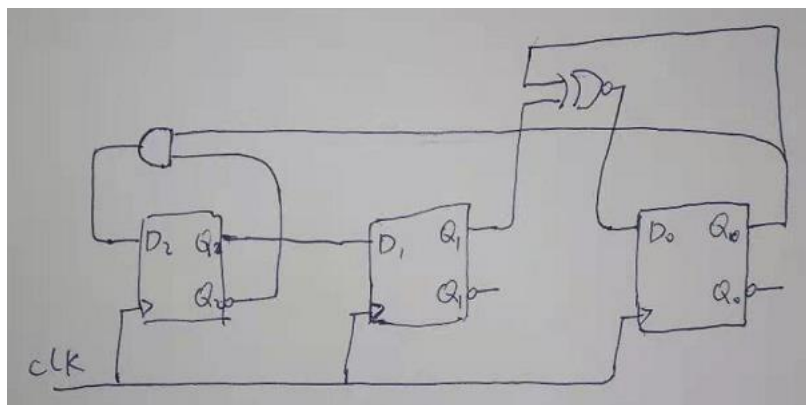(3) $D_2 = Q_2'Q_0$; $D_1 = Q_2$; $D_0 = Q_1Q_0 + Q_1'Q_0'$;



正确给出逻辑图得 5 分；否则正确给出一个驱动方程给 1 分。

得分

VI. Design a “0111010001” sequence generator with a 4-bit shift register 74x194. (18’)


- (1) Complete the Table 2 to realize the above sequence generator. Q3, Q2, Q1 and Q0 in Table 2 represent the corresponding signals in Figure 6. Choose the approach of minimal risk for unused states. [8’]
- (2) If Q0* is obtained by an 8-input, 1-bit multiplexer 74x151, please give the values of D0~D7 in Figure 6. [8’]
- (3) Give the values of the other signals or connect them in Figure 6 to make the circuit work properly. [2’]

答案及参考评分：

- (1) 每行 1 分，共 8 分；
- (2) 每输入端 1 分，共 8 分。
- (3) Y 连接至 LIN，1 分
- S1S0=10，1 分
- 其它端子连接不正确，适当扣分，扣完为止。

Table 2 Transition table

Q3	Q2	Q1	Q0	Q3*	Q2*	Q1*	Q0*
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	1
1	1	1	1	1	1	1	0

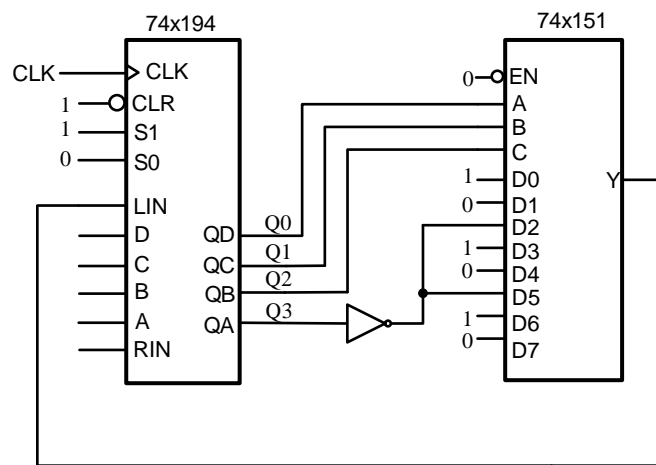

A3=B3	A2=B2	A1>B1	X	X	X	X	1	0	0
A3=B3	A2=B2	A1<B1	X	X	X	X	0	1	0
A3=B3	A2=B2	A1=B1	A0>B0	X	X	X	1	0	0
A3=B3	A2=B2	A1=B1	A0<B0	X	X	X	0	1	0
A3=B3	A2=B2	A1=B1	A0=B0	X	X	X	A>BIN	A<BIN	A=BIN